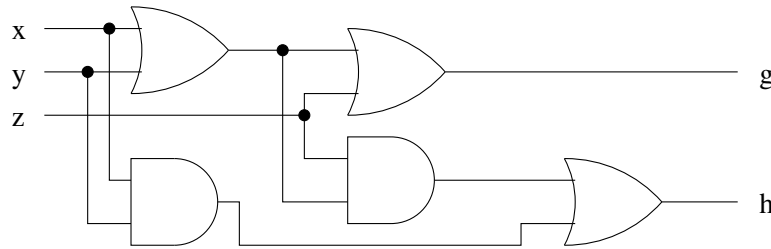


CMPT 295: Combinational Logic Questions

NOTE: In the following Boolean expressions, x' is another way of indicating “the complement of x .”

1. For the Boolean function $F(A, B, C) = AB'C + A'C' + AB$ find “algebraic” representations as follows:
 - (a) An equivalent representation using only AND and NOT.
 - (b) An equivalent representation using only OR and NOT.
2. Consider the function: $f(a, b, c) = (a'b'c' + a'b'c + ab'c + abc)'$
 - (a) Draw the logic diagram for the digital system whose functional specification is given by this expression.
 - (b) What is the dual of f ?
 - (c) Draw the logic diagram for the digital system whose functional specification is given by the dual of f .
3. Construct a **behavioral description** for the following circuit, providing your functional specification in 2 ways - algebraically and as a function table:




4. Implement the following function using only 3 AND gates and any NOT gates as required.

$$H(X, Y, Z) = X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z' + X \cdot Y' \cdot Z + X \cdot Y \cdot Z'$$


5. Simplify the following to an expression that can be implemented with as few gates as possible.:

$$\overline{A} \cdot \overline{C} + \overline{A} \cdot B \cdot C + \overline{B} \cdot C =$$

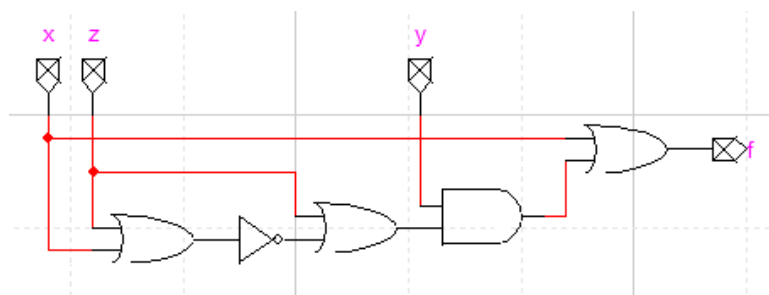6. Construct a simpler circuit for a function **f**, currently implemented as follows:



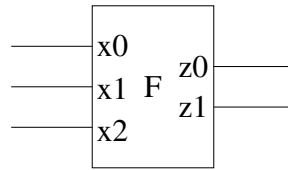7. A digital system has the following behavioral description:



x2	x1	x0	z1	z0
0	0	0	0	1
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

- Construct Boolean expressions for the functional specification of this system.
- Using the laws of Boolean algebra, obtain a simpler but equivalent functional specification using only AND, OR, and NOT.
- Draw the logic diagram from the simplified specification.