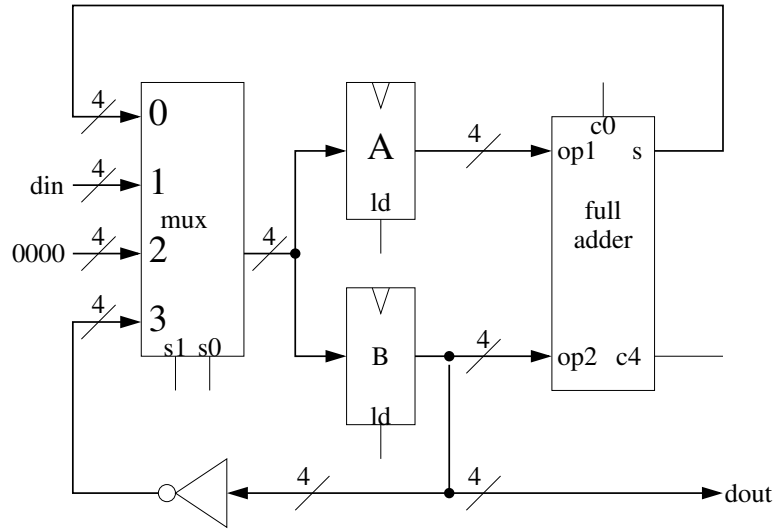


## Sample Sequential Circuit Questions

1. Consider the following logic diagram of a sequential system:




- (a) On the diagram, label all the control inputs only.
- (b) Propose a control word format for this system, indicating which control inputs are defined by which bit positions.
- (c) For each of the following tasks determine if it can be performed by a single  $\mu$ -instruction; that is, by a single control word assignment. If it can, then give the control word that will cause the task to be executed, using your control word format from question (b).
  - i.  $B \leftarrow A \text{ plus } B$
  - ii.  $A \leftarrow 0$
  - iii.  $A \leftarrow B'$
  - iv.  $B \leftarrow -B$
- (d) Without using data input port 1 of the MUX, Find a sequence of  $\mu$ -instructions, expressed as register transfer statements, that enable the sequential system to perform the following tasks:
 

HINT: How is the functional specification of an n-bit Full Adder expressed?

  - i.  $A \leftarrow 1$
  - ii.  $A \leftarrow -1$

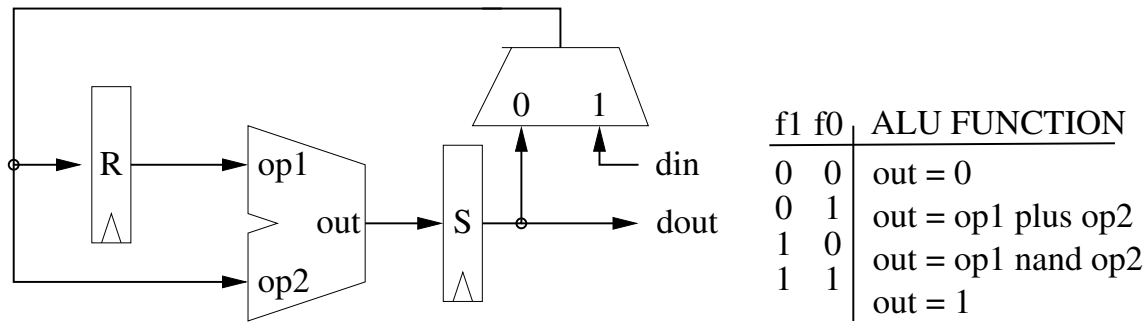2. A digital system is implemented by the following logic diagram:



R and S are storage registers.

- (a) On the logic diagram assign and label the control inputs to all devices as required.
- (b) Which of the following register transfer statements are  $\mu$ -instructions? For those that are, indicate what values the control inputs must have to achieve the desired effect. For those that are not, give a sequence of  $\mu$ -instructions that will result in the desired effect.
- $S \leftarrow 1$
  - $S \leftarrow R \text{ plus } 1$
  - $S \leftarrow -1$