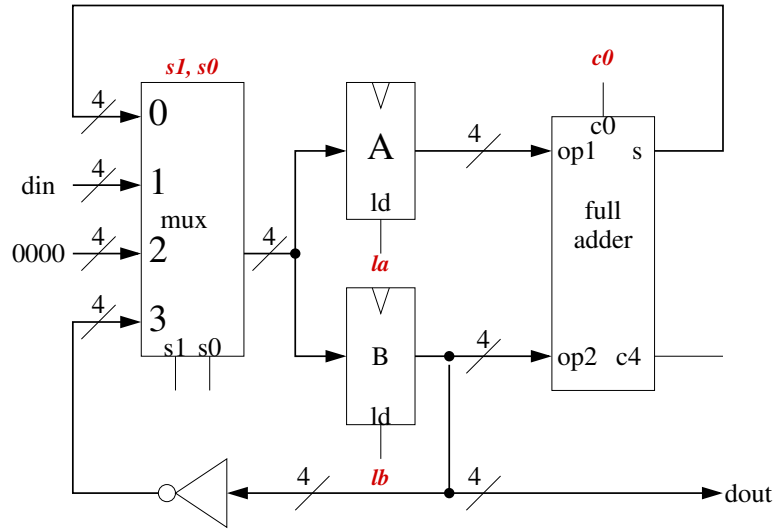


## Sample Sequential Circuit Questions SOLUTIONS

1. Consider the following logic diagram of a sequential system:



- (a) On the diagram, label all the control inputs only.
- (b) Propose a control word format for this system, indicating which control inputs are defined by which bit positions.

ANSWER:

s1	s0	la	lb	c0
4	3	2	1	0

- (c) For each of the following tasks determine if it can be performed by a single  $\mu$ -instruction; that is, by a single control word assignment. If it can, then give the control word that will cause the task to be executed, using your control word format from question (b).

i.  **$B \leftarrow A \text{ plus } B$**

ANSWER: Yes: 00010

ii.  **$A \leftarrow 0$**

ANSWER: Yes: 1010X

iii.  **$A \leftarrow B'$**

ANSWER: Yes: 1110X

iv.  **$B \leftarrow -B$**

ANSWER: No, it will take 2  $\mu$ -instructions

- (d) Without using data input port 1 of the MUX, Find a sequence of  $\mu$ -instructions, expressed as register transfer statements, that enable the sequential system to perform the following tasks:

HINT: How is the functional specification of an n-bit Full Adder expressed?


i.  $A \leftarrow 1$

ANSWER:  $A \leftarrow 0$   
 $B \leftarrow 0$   
 $A \leftarrow A \text{ plus } B \text{ plus } 1$

ii.  $A \leftarrow -1$

ANSWER:  $A \leftarrow 0$   
 $B \leftarrow 0$   
 $B \leftarrow A \text{ plus } B \text{ plus } 1$   
 $B \leftarrow B'$   
 $A \leftarrow A \text{ plus } B \text{ plus } 1$

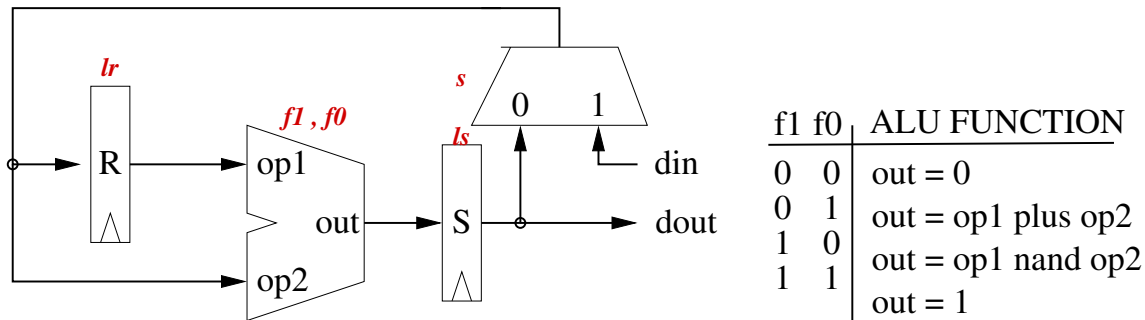2. A digital system is implemented by the following logic diagram:



R and S are storage registers.

- (a) On the logic diagram assign and label the control inputs to all devices as required.
- (b) Which of the following register transfer statements are  $\mu$ -instructions? For those that are, indicate what values the control inputs must have to achieve the desired effect. For those that are not, give a sequence of  $\mu$ -instructions that will result in the desired effect.

i.  $S \leftarrow 1$

ANSWER: Control word format: 

lr	f1	f0	ls	s
4	3	2	1	0

Control word: 0111X

ii.  $S \leftarrow R \text{ plus } 1$

ANSWER: Control word: 00111 (with  $din = 1$ )

iii.  $S \leftarrow R \text{ nand } S$

ANSWER: Control word: 01010

iv.  $S \leftarrow -1$

ANSWER:  $\mu$ -program:  $\frac{\mu\text{-instruction}}{S \leftarrow 0}$   
 $R \leftarrow S$   
 $S \leftarrow R \text{ nand } S$

OR

$\frac{\mu\text{-instruction}}{S \leftarrow 1}$   
 $R \leftarrow S$   
 $S \leftarrow R \text{ nand } S$   
 $R \leftarrow S$   
 $S \leftarrow 1$   
 $S \leftarrow R \text{ plus } S$